

# Datapath Design

# Timing Design in Digital Systems


# One clock

---

- ❑ One clock, one edge; Flip-flops only
  - For your design (at least for each module) use one clock source and only one edge of that clock
  - Only use edge-triggered flip-flops
- ❑ Why?
  - Moving data between different clock domains requires careful timing design and synthesis “scripting”
- ❑ If you need multiple clocks in your design
  - Make them related by a powers of 2
    - E.g 50, 100 and 200 MHz
  - Consider one clock per module
- ❑ Consider resynchronizing using flip-flops between clock domains



 
# General Approach to Timing Design

- ❑ In general, all signals start and end in registers every clock period





# Clock Level Timing

## □ Example

   



# Clock Level Timing

## □ Example

  



# Clock Level Timing

## □ Example

  

# Clock Level Timing


## □ Example

  


 
# Critical Path

- ❑ The clock speed is determined by the slowest feasible path between registers in the design
  - Often referred to as “the critical path”



Critical path is longer  
with increased *logic  
depth* (# gates in series)


# Synchronous Clock Distribution

---

- ❑ The goal of clock tree is for the clock to arrive at every leaf node at the same time
- ❑ Usually designed after synthesis: Matched buffer, matched capacitance loads
- ❑ Common design method:
  - “H tree”
  - Clock tree done after design
  - Balance RC delays
  - Balance buffer delays
 
# Clock skew and jitter

- ❑ Clock skew = systematic clock edge variation between sites
  - Mainly caused by delay variations introduced by manufacturing variations
  - Random variation
- ❑ Clock jitter = variation in clock edge timing between clock cycles
  - Mainly caused by noise



# Flip-Flop based design

## ❑ *Edge triggered D-flip-flop*

- Q becomes D after clock edge

## ❑ *Set-up time*


- Data can not change no later than this point before the clock edge.

## ❑ *Hold time*

- Data can not change during this time after the clock edge.

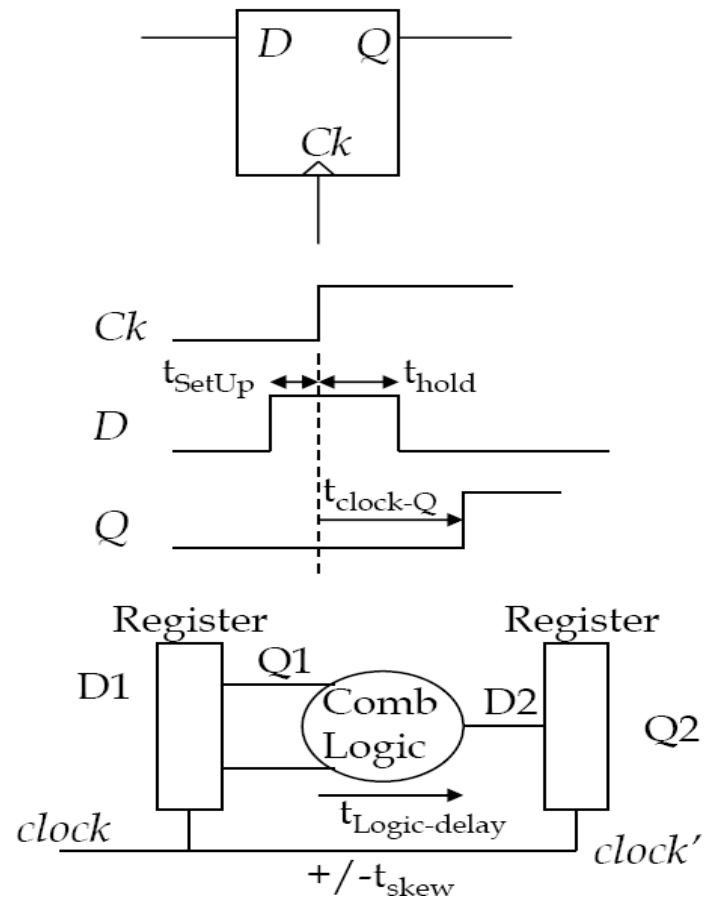
## ❑ *$t_{\text{clock-Q}}$*

- Delay on output (Q) changing from positive clock edge



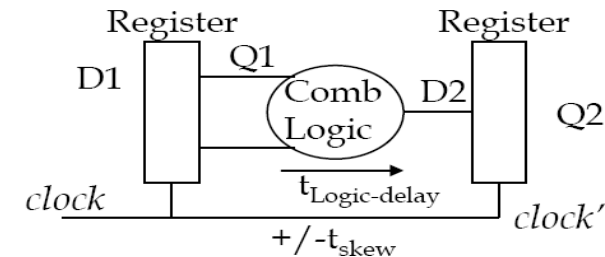
# Preventing Set-Up Violations

- ❑ **Set-up violation:** Logic is too slow for the correct logic value to arrive at the inputs to the register on the right before one set-up time before the clock edge



- ❑ Constraint to prevent this:
 
$$t_{\text{clock}} \geq t_{\text{clock-Q-max}} + t_{\text{logic-max}} + t_{\text{set-up}} + t_{\text{skew}}$$




Violation  
if D2 changes  
after this time

The amount of time required to turn '>' into '=' is referred to as **timing slack**
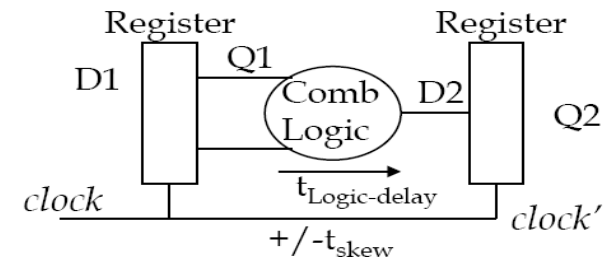
# Preventing hold Violations

- ❑ Hold violations occur when race-through is possible
  - What is the worst case for clock'?
  - **Clock' arrives after clock → more time for D2 to change**
  - sometimes we have to insert logic to prevent hold violations
- ❑ Constraint to prevent hold violations:  
$$t_{hold} + t_{skew} \leq t_{clock-Q-min} + t_{logic-min}$$





# Preventing hold Violations

- Hold violations occur when race-through is possible
  - What is the worst case for clock'?
  - Clock' arrives after clock → more time for D2 to change
  - sometimes we have to insert logic to prevent hold violations

- Constraint to prevent hold violations:
 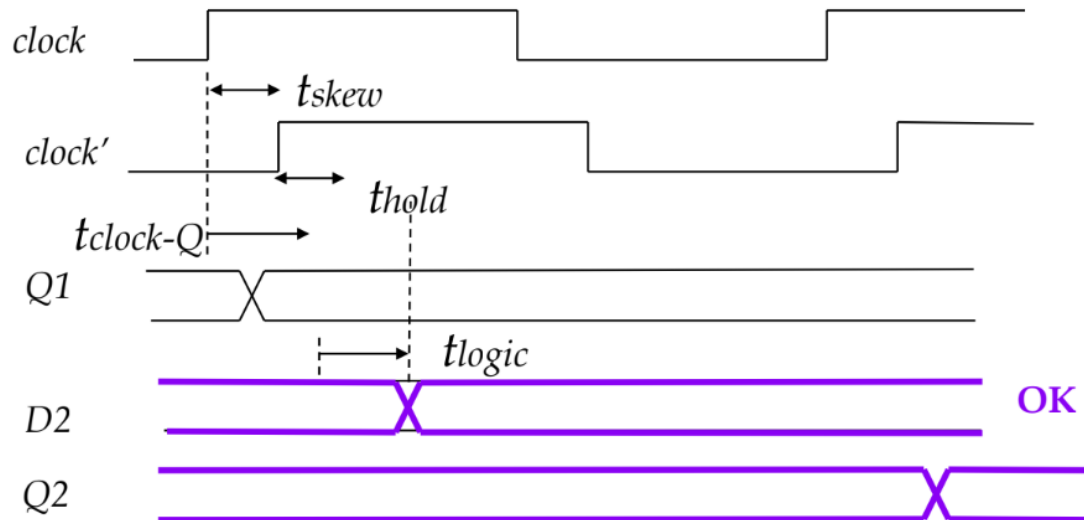
$$t_{hold} + t_{skew} \leq t_{clock-Q-min} + t_{logic-min}$$





# Preventing hold Violations

- Hold violations occur when race-through is possible
  - What is the worst case for clock'?
  - Clock' arrives after clock → more time for D2 to change
  - sometimes we have to insert logic to prevent hold violations

- Constraint to prevent hold violations:
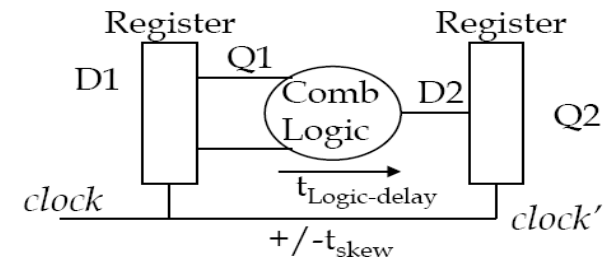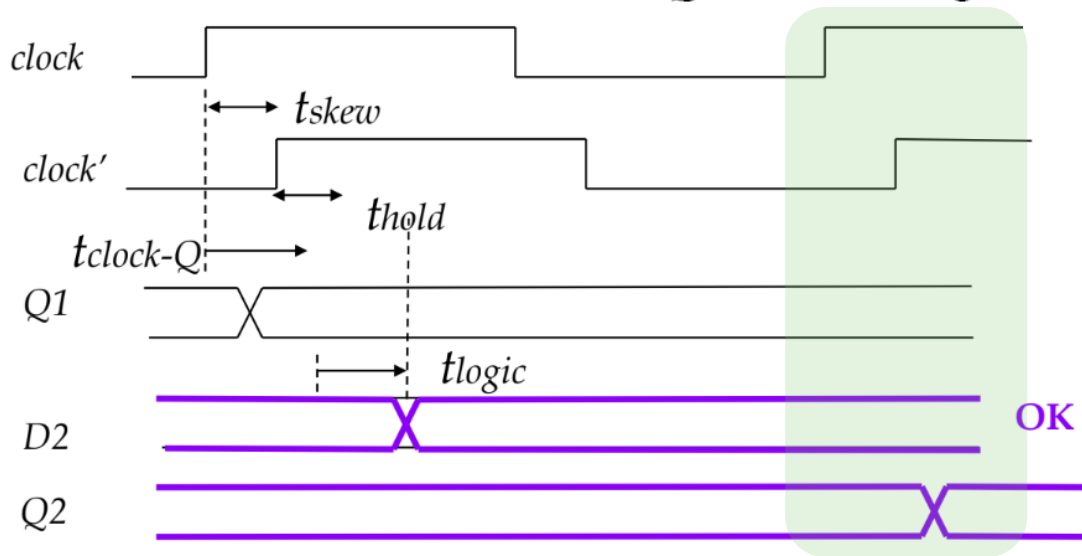
$$t_{hold} + t_{skew} \leq t_{clock-Q-min} + t_{logic-min}$$







# Preventing hold Violations

- Hold violations occur when race-through is possible
  - What is the worst case for clock'?
  - Clock' arrives after clock → more time for D2 to change
  - sometimes we have to insert logic to prevent hold violations

- Constraint to prevent hold violations:
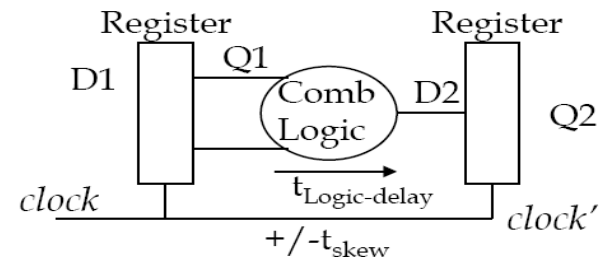 
$$t_{hold} + t_{skew} \leq t_{clock-Q-min} + t_{logic-min}$$





If D2 changes before this time:  
Incorrect Q2 or race through

# Preventing hold Violations

- Hold violations occur when race-through is possible
  - What is the worst case for clock'?
  - Clock' arrives after clock → more time for D2 to change
  - sometimes we have to insert logic to prevent hold violations

- Constraint to prevent hold violations:

  
$$t_{hold} + t_{skew} \leq t_{clock-Q-min} + t_{logic-min}$$



If D2 changes before this time:  
Incorrect Q2 or race through
 
# Preventing set-up/hold Violations

- ❑ Example: what is the fastest clock frequency? Is there potential for a hold violation?



min : typ : max

$T_{\text{clock-Q}} = 3 : 4 : 5$

$T_{\text{NOR}} = 1 : 2 : 3$


$T_{\text{su\_max}} = 1$

$T_{\text{hold\_max}} = 2$

$T_{\text{skew}} = 1 \text{ ns}$

# Preventing set-up/hold Violations

 - Example: what is the fastest clock frequency? Is there potential for a hold violation?



min : typ : max

$T_{\text{clock-Q}} = 3 : 4 : 5$

$T_{\text{NOR}} = 1 : 2 : 3$

$T_{\text{su\_max}} = 1$


$T_{\text{hold\_max}} = 2$

$T_{\text{skew}} = 1 \text{ ns}$

$$\begin{aligned} \text{Setup: } t_{\text{clock}} &\geq t_{\text{clock-Q-max}} + t_{\text{logic-max}} + t_{\text{setup}} + t_{\text{skew}} \\ &= 5 + (3 + 3) + 1 + 1 \text{ ns} = 13 \text{ ns} \rightarrow 76 \text{ MHz} \end{aligned}$$

# Preventing set-up/hold Violations

 - Example: what is the fastest clock frequency? Is there potential for a hold violation?




min : typ : max  
 $T_{\text{clock-Q}} = 3 : 4 : 5$   
 $T_{\text{NOR}} = 1 : 2 : 3$   
 $T_{\text{su\_max}} = 1$   
 $T_{\text{hold\_max}} = 2$   
 $T_{\text{skew}} = 1 \text{ ns}$

Setup:  $t_{\text{clock}} \geq t_{\text{clock-Q-max}} + t_{\text{logic-max}} + t_{\text{setup}} + t_{\text{skew}}$   
 $= 5 + (3 + 3) + 1 + 1 \text{ ns} = 13 \text{ ns} \rightarrow 76 \text{ MHz}$



Hold: Is  $t_{\text{hold}} + t_{\text{skew}} \leq t_{\text{clock-Q-min}} + t_{\text{logic-min}}$  ?  
 $2 + 1 \leq 3 + 1 \rightarrow \text{No we don't have a hold violation}$
 
# What can happen with a Timing Violation

- D changes outside setup & hold  $\rightarrow t_{\text{clock-Q}}$  is correct




  - D changes during setup & hold  $\rightarrow t_{\text{clock-Q}}$  is longer than specified, or Q doesn't transition correctly




 
# What can happen with a Timing Violation

- D changes outside setup & hold  $\rightarrow t_{\text{clock-Q}}$  is correct



  
- D changes during setup & hold  $\rightarrow t_{\text{clock-Q}}$  is longer than specified, or  $Q$  doesn't transition correctly




*Incorrect timing in the next logic stage*
 
# What can happen with a Timing Violation


- D changes outside setup & hold  $\rightarrow t_{\text{clock-Q}}$  is correct



 - D changes during setup & hold  $\rightarrow t_{\text{clock-Q}}$  is longer than specified, or  $Q$  doesn't transition correctly



 *Incorrect timing in the next logic stage*




*Logic Failure*



 
# What can happen with a Timing Violation

- ❑ D changes outside setup & hold  $\rightarrow t_{\text{clock-Q}}$  is correct




- ❑ D changes during hold

 

 
# What can happen with a Timing Violation

- ❑ D changes outside setup & hold  $\rightarrow t_{\text{clock-Q}}$  is correct



- ❑ D changes during hold

 

*Q correct, wrong cycle  
Racethrough*

# Timing Tables



Timing Constraints at 25°C, 1.8V, Typical Process

Pin	Requirement	Interval (ns)			
		XL	X1	X2	X4
D	setup $\uparrow$ $\rightarrow$ CK	0.04	0.06	0.06	0.06
	setup $\downarrow$ $\rightarrow$ CK	0.10	0.15	0.15	0.14
	hold $\uparrow$ $\rightarrow$ CK	-0.02	-0.04	-0.04	-0.03
	hold $\downarrow$ $\rightarrow$ CK	0.01	-0.04	-0.04	-0.04
CK	minpwh	0.18	0.18	0.18	0.18
	minpwl	0.25	0.25	0.25	0.25



## Timing Tables

Delays at 25°C, 1.8V, Typical Process

Description	Intrinsic Delay (ns)				$K_{load}$ (ns/pF)			
	XL	X1	X2	X4	XL	X1	X2	X4
CK $\rightarrow$ Q $\uparrow$	0.219	0.197	0.180	0.155	5.696	4.288	2.261	1.139
CK $\rightarrow$ Q $\downarrow$	0.179	0.166	0.153	0.132	3.406	2.469	1.234	0.611
CK $\rightarrow$ QN $\uparrow$	0.238	0.221	0.196	0.179	6.239	4.518	2.259	1.138
CK $\rightarrow$ QN $\downarrow$	0.304	0.280	0.251	0.219	3.342	2.444	1.219	0.605
  
# Delay Metric

- ❑ Usual Metric for delay:
  - Fanout of 4 inverter delay: FO4
- ❑ Estimating FO4:
  - Typical  $\sim 360 \times L_{\text{gate}}$  (ps)
  - Worst Case  $\sim 600 \times L_{\text{gate}}$  (ps)
  - E.g. In a 28nm process FO-4  $\leq 16.8$  ps




# Delay Metric

---

- ❑ Usual Metric for delay:
  - Fanout of 4 inverter delay: FO4
- ❑ Estimating FO4:
  - Typical  $\sim 360 \times L_{\text{gate}}$  (ps)
  - Worst Case  $\sim 600 \times L_{\text{gate}}$  (ps)
  - E.g. In a 28nm process FO-4  $\leq 16.8$  ps
- ❑ Example Delays:
  - Inverter = FO-4
  - 2-input NAND gate = 2FO4
  - 1-bit adder = 10 FO4
  - 2-input Multiplexer = 4 FO4
  - Flip-flop  $t_{\text{cp-Q}}$  = 4 FO4
  - Flip-flop  $t_{\text{su}} / t_{\text{h}}$  = 2 FO4
  - Clock skew = 4 FO4
  - Clock jitter = 2 FO4

 
# Improving Timing Performance

- ❑ Example 1 : Benefits of Pipelining and Parallelism
  - If  $t_{\text{comparator}} = 20 \text{ FO4}$ , what is the clock period?  
(Use values on previous page)


 
# Improving Timing Performance


- ❑ Example 1 : Benefits of Pipelining and Parallelism
  - If  $t_{\text{comparator}} = 20 \text{ FO4}$ , what is the clock period?  
(Use values on previous page)



$$\begin{aligned} T_{cp} &= t_{ck-Q} + t_{logic} + t_{su} + t_{skew} \\ &= 4 + 3 \cdot 20 + 2 + 4 \\ &= 70 \text{ FO4} \end{aligned}$$
 
# Improving Timing Performance


- ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?
- ❑ What is the drawback?





 
# Improving Timing Performance

- ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?  $4+20+2+4=30FO4$  (2.3x not 3x)
- ❑ What is the drawback?



 
# Improving Timing Performance

- ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?  $4+20+2+4=30FO4$  (2.3x not 3x)
- ❑ What is the drawback? Increased latency, additional circuit



 
# Improving Timing Performance

- ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?  $4+20+2+4=30FO4$  (2.3x not 3x)
- ❑ What is the drawback? Increased latency, additional circuit



 
# Improving Timing Performance

- ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?  $4+20+2+4=30FO4$  (2.3x not 3x)
- ❑ What is the drawback? Increased latency, additional circuit



 
# Improving Timing Performance

- ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?  $4+20+2+4=30FO4$  (2.3x not 3x)
- ❑ What is the drawback? Increased latency, additional circuit



 
# Improving Timing Performance

- ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?  $4+20+2+4=30FO4$  (2.3x not 3x)
- ❑ What is the drawback? Increased latency, additional circuit




 - ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?  $4+20+2+4=30FO4$  (2.3x not 3x)
- ❑ What is the drawback? Increased latency, additional circuit


 
# Improving Timing Performance

- ❑ Replace with a pipelined version
- ❑ Operation
  - Adding pipeline stages reduces the clock period
  - Overlapping computations at the same time
- ❑ Delay improvement?  $4+20+2+4=30FO4$  (2.3x not 3x)
- ❑ What is the drawback? Increased latency, additional circuit




Keep synchronicity at each stage they keep the different waves (colors) together



 
# Improving Timing Performance

- ❑ Replace with:
  - Parallelism at logic level
- ❑ Clock Period?
  -



 
# Improving Timing Performance

- ❑ Replace with:
  - Parallelism at logic level
- ❑ Clock Period?  $4 + 2 \cdot 20 + 2 + 4 = 50 \text{ FO4}$ 
  -


 
# Improving Timing Performance

- ❑ Replace with:
  - Parallelism at logic level
- ❑ Clock Period?  $4 + 2 \cdot 20 + 2 + 4 = 50 \text{ FO4}$ 
  - No increase in area




# Retiming

- ❑ Impact of critical paths can often be reduced by retiming or rebalancing a design

- Before:



- After:

 

# Retiming


- ❑ Impact of critical paths can often be reduced by retiming or rebalancing a design

- Before:



$$T_{cp} = 4 + (20 + 5) + 2 + 4 = 35 \text{ FO4}$$

- After:

 

# Retiming


- Impact of critical paths can often be reduced by retiming or rebalancing a design

- Before:



$$T_{cp} = 4 + (20 + 5) + 2 + 4 = 35 \text{ FO4}$$

- After:

 

$$T_{cp} = 4 + (20) + 2 + 4 = 30 \text{ FO4}$$


# Timing in CAD Flow

---

- ❑ During synthesis
  - Tool calculates path delays under worst-case delay conditions
  - Determines critical path
  - Moves logic to a faster path if setup violation predicted
- ❑ After synthesis:
  - Perform Static Timing Analysis
  - Determine no setup violations exist under worst case conditions
  - Determine no hold violations exist under best case conditions
- ❑ After place and route:
  - Perform Timing Analysis
  - i.e. Run timing verification tools on netlist with actual delays
  - Back-annotate actual delays to netlist from later tools
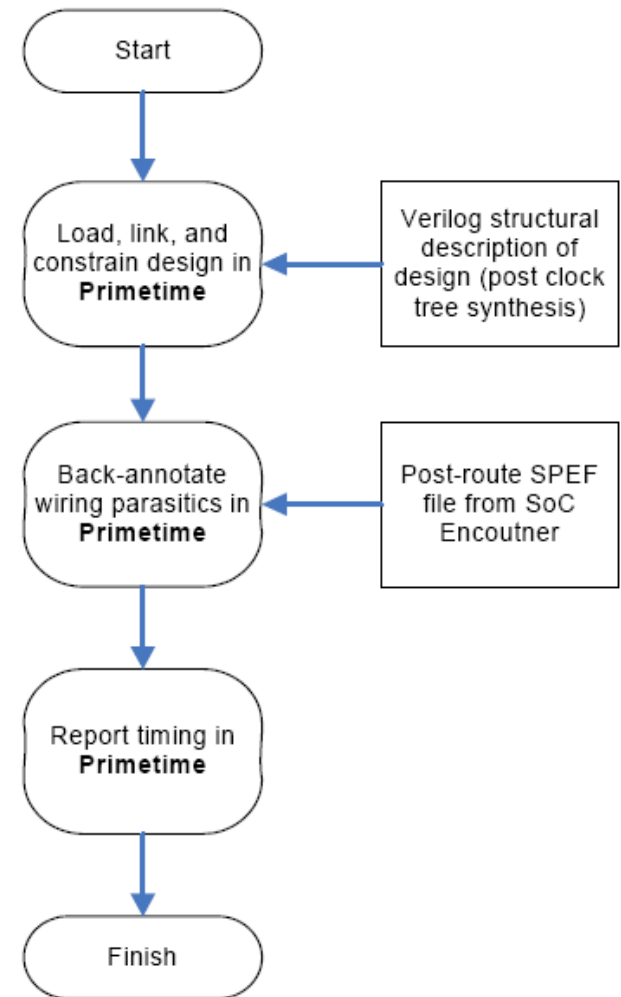
# Initial Delay Estimation Flow

- ❑ Primetime: Gate-level static timing analysis tool
  - Report timing for critical path
- ❑ Back-annotate wire parasitics for more accuracy
  - SPEF file from place and route tool





# **How to Design Complex Digital Systems**

# Steps in High Level Design

---

- ❑ Determine MicroOperations to be performed on datapath units
  - e.g. adds, subtracts, multiplies, memory references, etc.
- ❑ Design datapath units to perform these operations efficiently
  - Design to RTL level
- ❑ Identify control points
  - Control lines
  - Status lines
- ❑ Determine reset/start/stop/transition actions
  - Especially global reset strategy

# Steps in High Level Design



---

- Determine control sequence
  - Generally MicroOp sequence required to perform overall task
  - Gives sequence of control events and status line responses
- Determine control strategy
  - Mix of FSMs and/or counters
- Verify before coding

# Control Strategies

 
 
## ❑ Counters:

- Takes machine through a linear sequence of states with few decisions along the way


  
## ❑ FSMs


- Permits branches in control decision chain



# Control Strategies
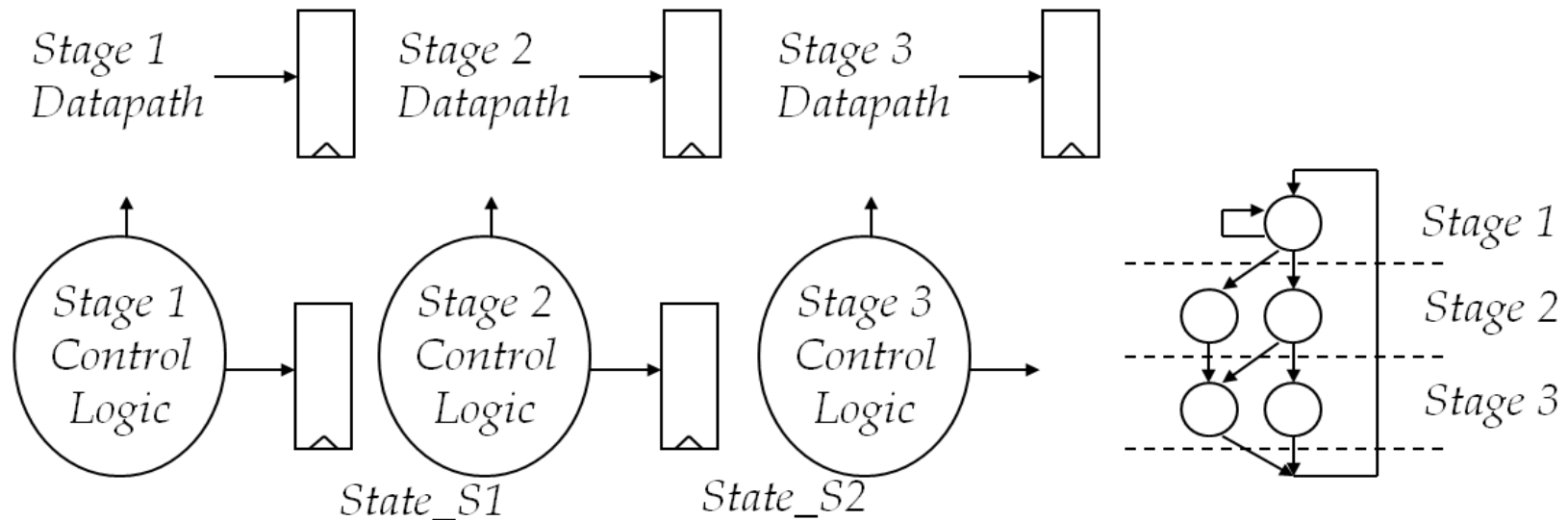
## ❑ Pipeline Control

- In a sense, an “unrolled” FSM – each stage does one step (or one of several parallel steps) in an FSM; state information communicated between stages



# Reset

- ❑ Reset is a global signal that the designer can not modify
- ❑ It is generally asserted on power up or a “hard” reset
- ❑ It is used to start the machine in a “known” state
- ❑ Thus it must be distributed to
  - All FSMs
  - Selected counters
  - Selected status registers



# Achieving Efficiency

---

## ❑ High level tradeoffs:

- Parallelism
- Pipelining
- Optimizing the critical resource
  - E.g. Memory bandwidth
- Keep resources busy
  - If a resource is idle can it be shared?
  - Goal : Everything is used every clock cycle

## ❑ Algorithmic Optimizations

- E.g. Algorithms that avoid DRAM accesses
  - e.g. Compress table onto SRAM
- Exploiting common algorithms in Computer Science
  - e.g. Hash tables for matches
  - e.g. Shift instead of  $\times 2 / 2$

# Achieving Efficiency

---

- ❑ Think hardware (area and delay):
  - Avoid large FSMs
  - Count the large units (\* + memories, etc.)
  - Avoid high-fanout signals
  - Avoid priority logic
  - Structure arithmetic for speed
    - E.g. CLA instead of ripple carry
- ❑ Exploit existing Intellectual Property



# Achieving Efficiency

---

- ❑ Synopsys, and others, provide libraries of carefully optimized design blocks to use – called “Design Ware”
  - Libraries include: Arithmetic, Advanced Math, DSP, Control, Sequential, and Fault Tolerant
  - For  $+$ ,  $-$ ,  $*$ ,  $\geq$ ,  $\leq$ ,  $>$ , and  $<$ , design ware is automatically used
  - More complex cells must be inferred via a procedure call, e.g. cosine

# Achieving Efficiency

---

- ❑ Synopsys, and others, provide libraries of carefully optimized design blocks to use – called “Design Ware”

```
module trigger (angle, cos_out);  
    parameter wordlength1 = 8, wordlength2 = 8;  
    input [wordlength1-1:0] angle;  
    output [wordlength2-1:0] cos_out;  
    // passes the widths to the cos function  
    parameter angle_width = wordlength1, cos_width = wordlength2;  
    `include "synopsys_syn/dw/sim_ver/DW02_cos_function.inc"  
    wire [wordlength2-1:0] cos_out;  
    // infer DW02_cos  
    assign cos_out = cos(angle);  
endmodule
```

# **Complex Design Example**

# “Mantras”


---

1. One clock, one edge, flip-flops only
2. Design BEFORE coding
3. Behavior implies function
4. Clearly separate control and datapath



 
# Design Example

- ❑ Motion Estimator
- ❑ Task: Detect blocks of video data in successive frames that are related only via a translation
  - Digital Video is captured as blocks of 16x16 pixels
  - Want to determine if block has moved largely unchanged
    - If true can transmit motion vector rather than block
    - Permits high level of compression
  - Example (4x4 block)



Reference Block in  
Frame 1

 

“Draw block” with  
motion vector (1,2)  
in frame 2

# Search Algorithm

Describe for 16x16 reference block:


1. Move a window the size of the reference block over search space in the second frame
2. For each window location (i,j) determine the distortion vector

$$D(i, j) = \sum_{m=0}^{15} \sum_{n=0}^{15} |r_{m,n} - S_{m+i, N+j}|$$

3. Maintain the best distortion and appropriate motion vector produced so far.
- For Example (4x4 block):



Reference  
Block in  
Frame 1

 

Search window  
in frame 2

Search Block Location (i,j)=(-3,3)  
D=3 (3 pixels different in this B&W  
example)

Original Location of Reference Block in  
Frame 1

# System Requirements

---

- ❑ System Requirements:
  - 16x16 Reference Block
  - 31x31 Search Window
  - Each stored in one two-read-ported memory
    - In reality one memory per frame
  - Grey-scale coded pixels (8 bits/block)
  - 4096 reference blocks in a frame
  - Conduct search at 15 frames per second
    - (Encoding does not have to be real time)
  - Clocks available : 130, 260 MHz
  - 0.25  $\mu\text{m}$  CMOS library

# Step 1 : System Design

---

## Elements to thinking:

- ❑ Bottom-up design
  - Determine critical bottlenecks (paths & other bottlenecks)
- ❑ Top-down design
  - Determine use of pipelining and parallelism to meet performance constraints

$$D = D + |r_{mn} - S_{m+i, N+j}|$$


## Critical Bottlenecks:

- ❑ Elemental Arithmetic Operation (add-accumulate):
  - Design, synthesize → Can operate at 260 MHz with some timing margin left over
- ❑ Memories:
  - Single access per clock cycle


 
# ... System Design

- ❑ Top Down Design
- ❑ Number of add-accumulates per clock cycle:
  - 4096 blocks per 1/15 of a second
  - $(31-15) \times (31-15) = 256$  searches/block
  - $16 \times 16 = 256$  add-accumulates per search
  - $\rightarrow 4096 \times 15 \times 256 \times 256 = 4.027E9$  add-accumulates/second
  - At 260 MHz  $\rightarrow$  At least 16 adders in parallel ( $4027/260 = 15.5$ )
- ❑ Searches/block [(4x4) on (10x10) example]:





7 searches per column  
7 searches per row  
 $(10-3) \times (10-3)$  total searches

# ...System Design

## □ First Attempt


- Assign one search per Accumulator

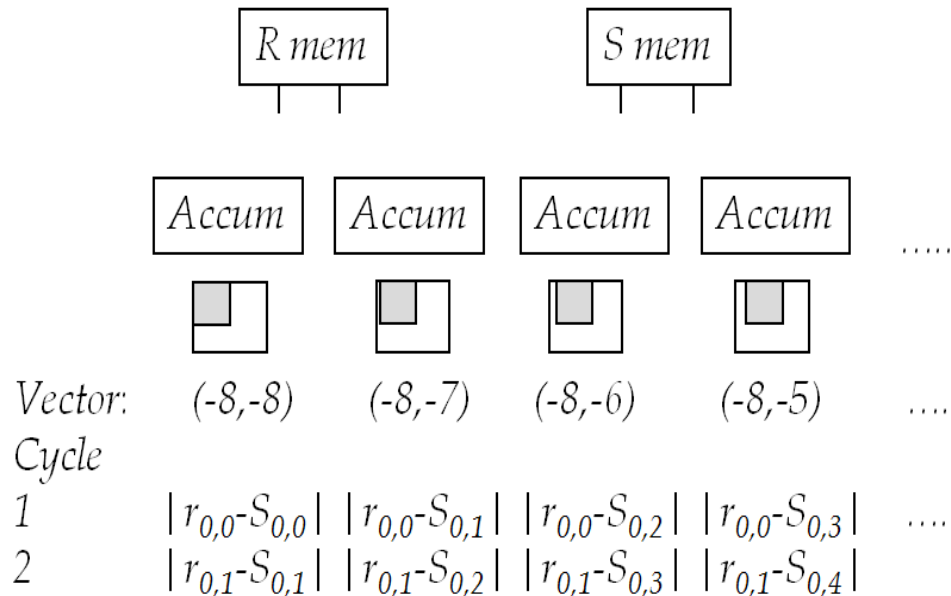 

# ...System Design

## □ First Attempt



- Assign one search per Accumulator

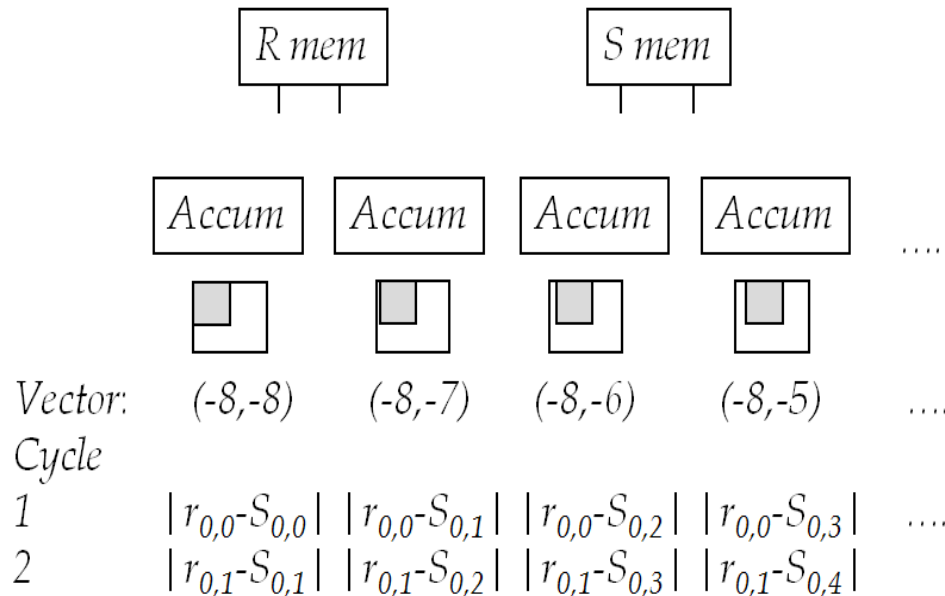

**Problem: Requires 16 port  
S memory**
 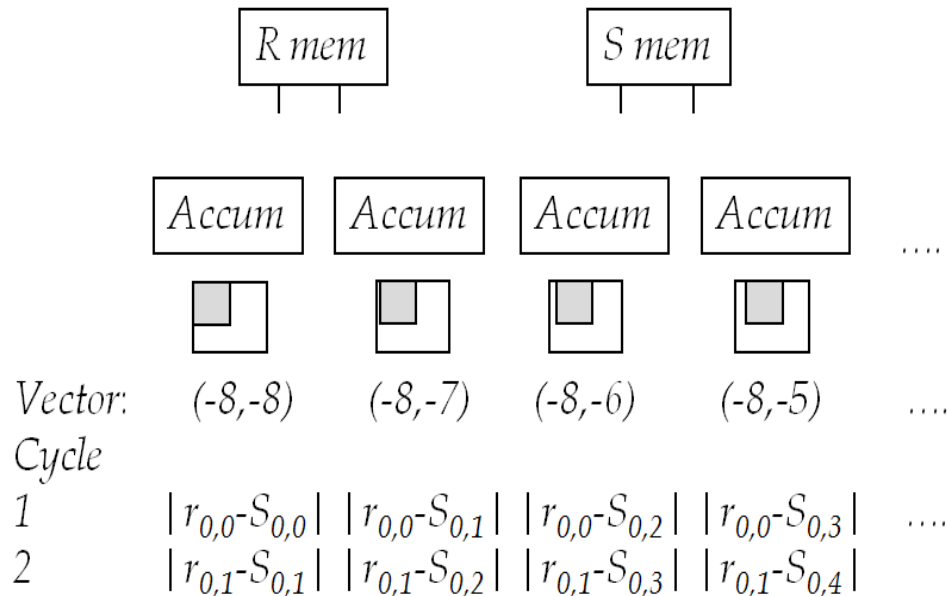
# ... System Design



- ❑ Second Attempt:
  - Stagger Startup of Accumulators



**Problem: Requires 16 port S memory**
 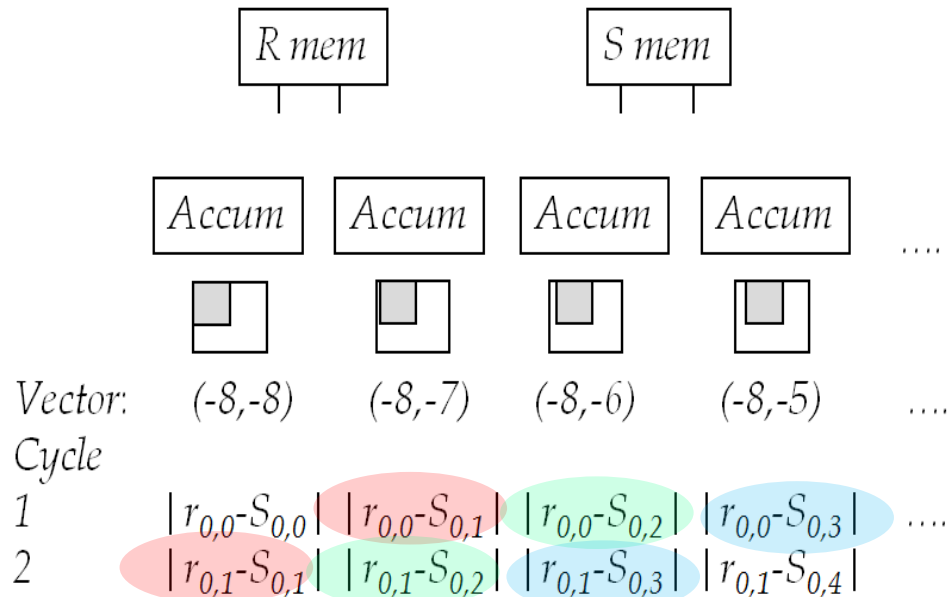
# ... System Design


- ❑ Second Attempt:
  - Stagger Startup of Accumulators



**Problem: Requires 16 port S memory**
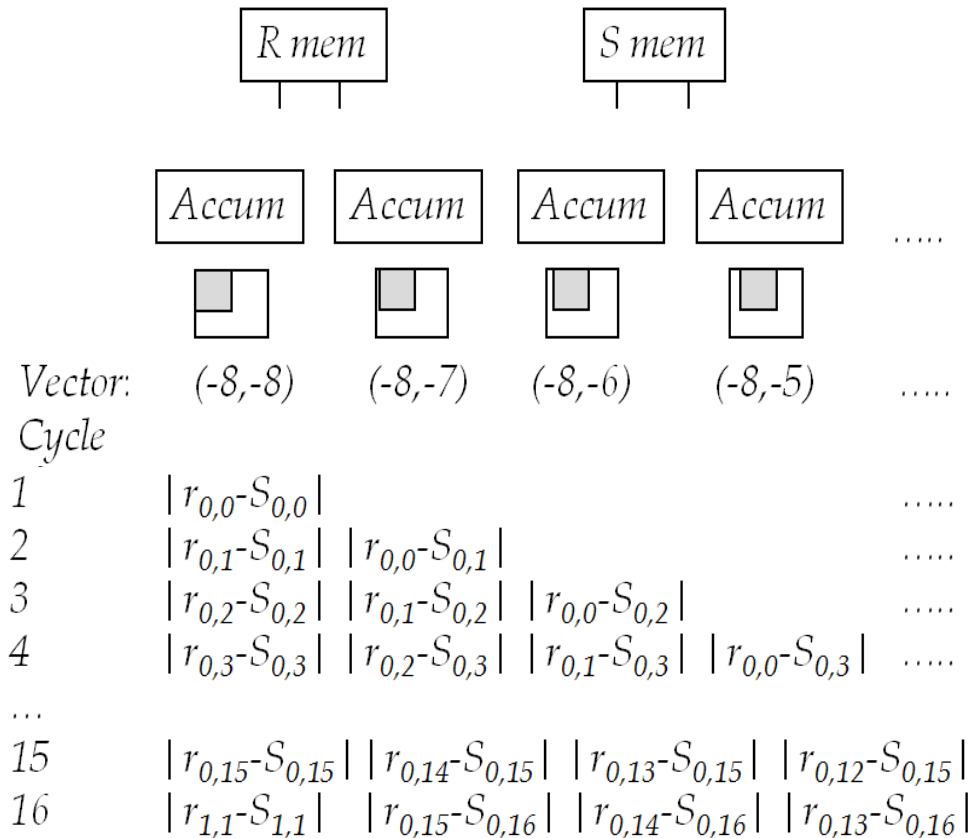
# ... System Design


- ❑ Second Attempt:
  - Stagger Startup of Accumulators



# ... System Design

- ❑ Second Attempt:
  - Stagger Startup of Accumulators


**Problem: Requires 16 port  
R memory**

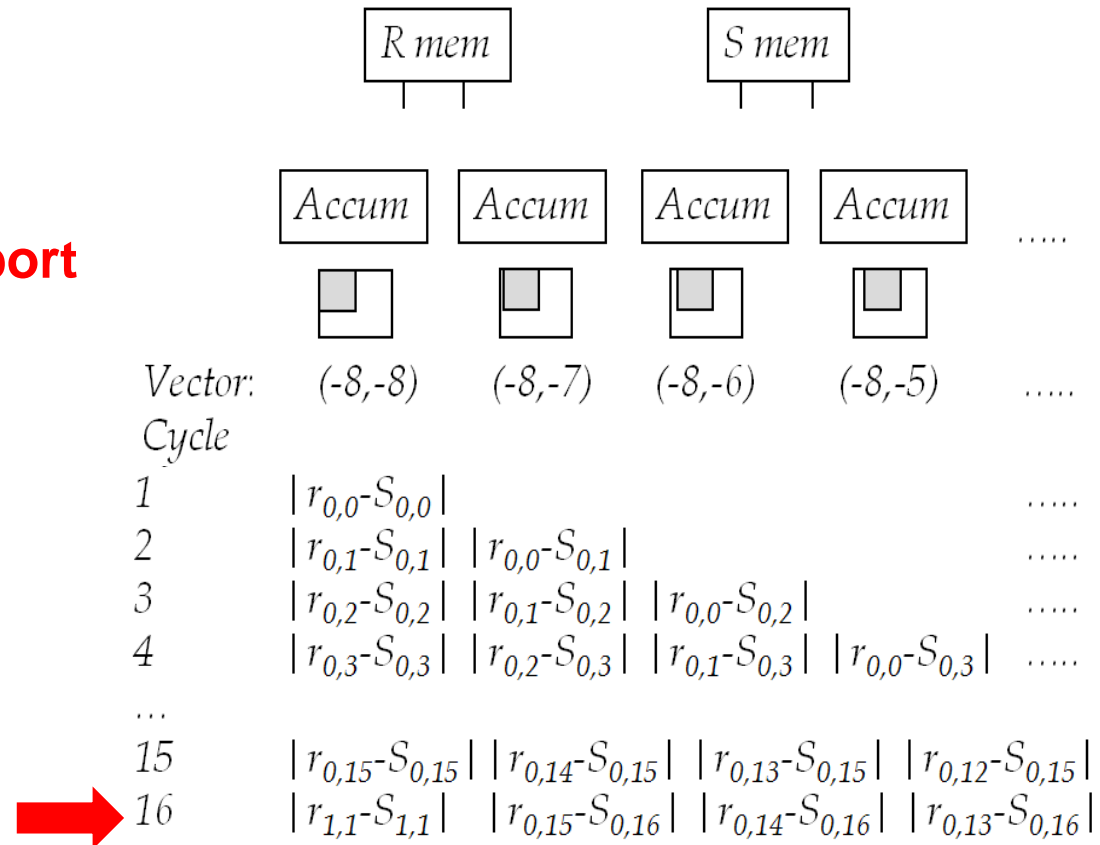

# ... System Design

- ❑ Second Attempt:
  - Stagger Startup of Accumulators

**Problem: Requires 16 port R memory**

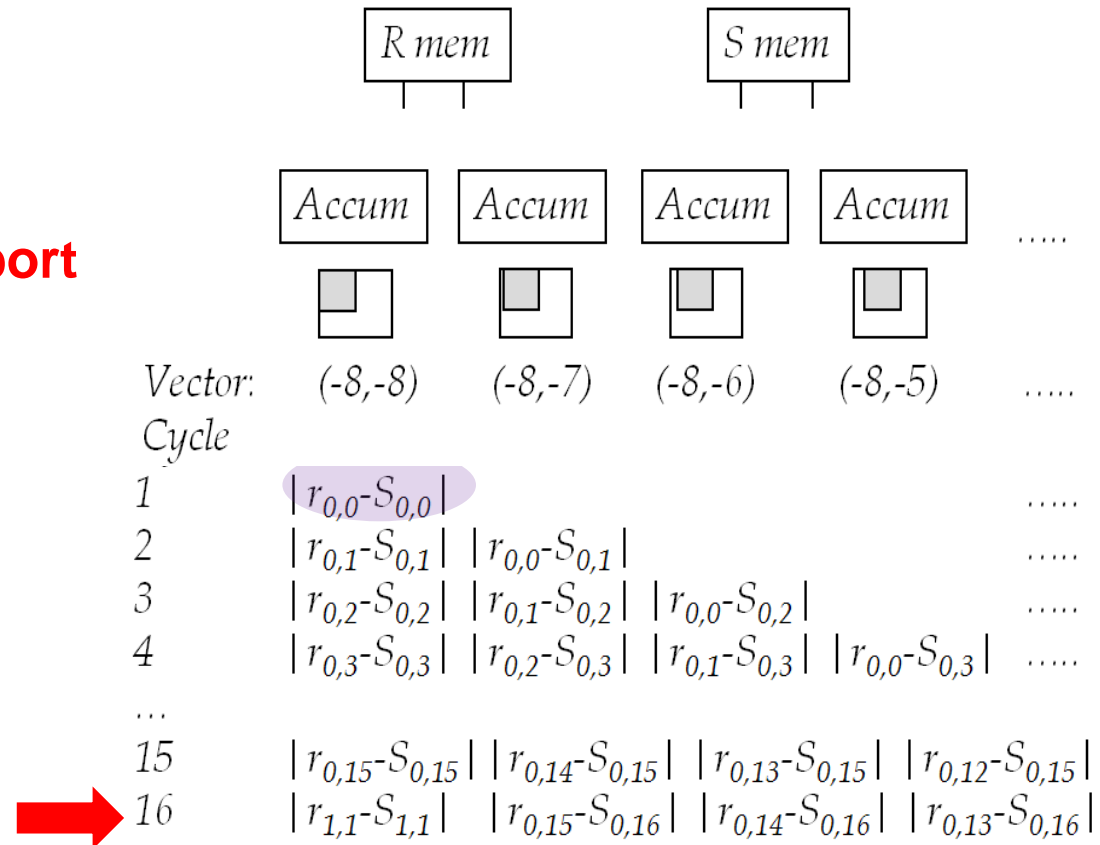




# ... System Design

- ❑ Second Attempt:
  - Stagger Startup of Accumulators


**Problem: Requires 16 port  
R memory**

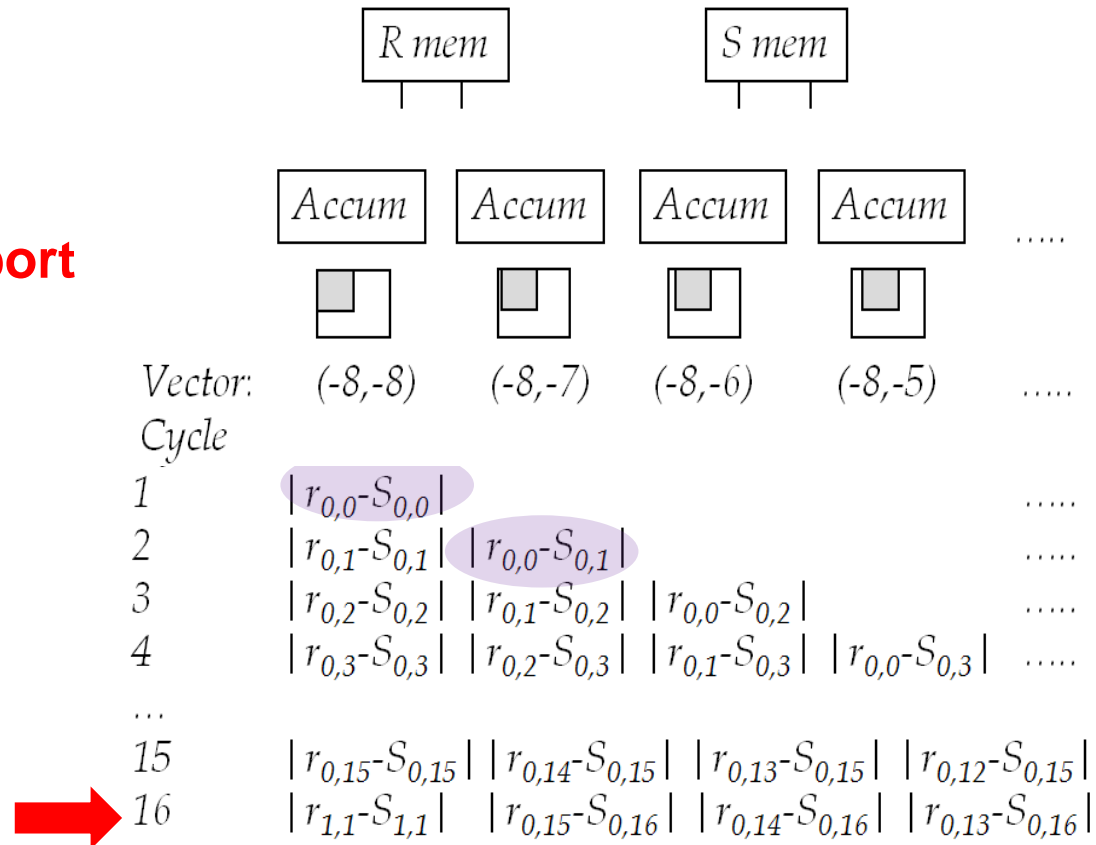

# ... System Design

- ❑ Second Attempt:
  - Stagger Startup of Accumulators


**Problem: Requires 16 port  
R memory**

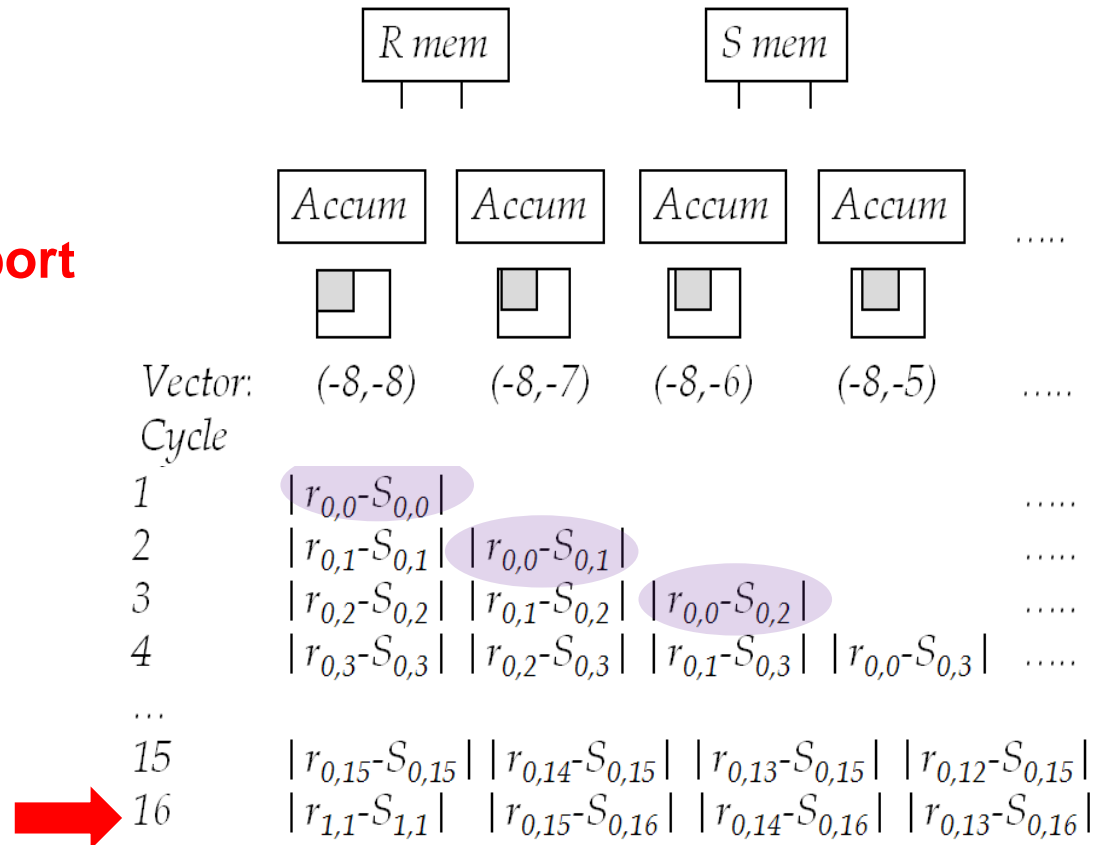

# ... System Design

- ❑ Second Attempt:
  - Stagger Startup of Accumulators


**Problem: Requires 16 port R memory**

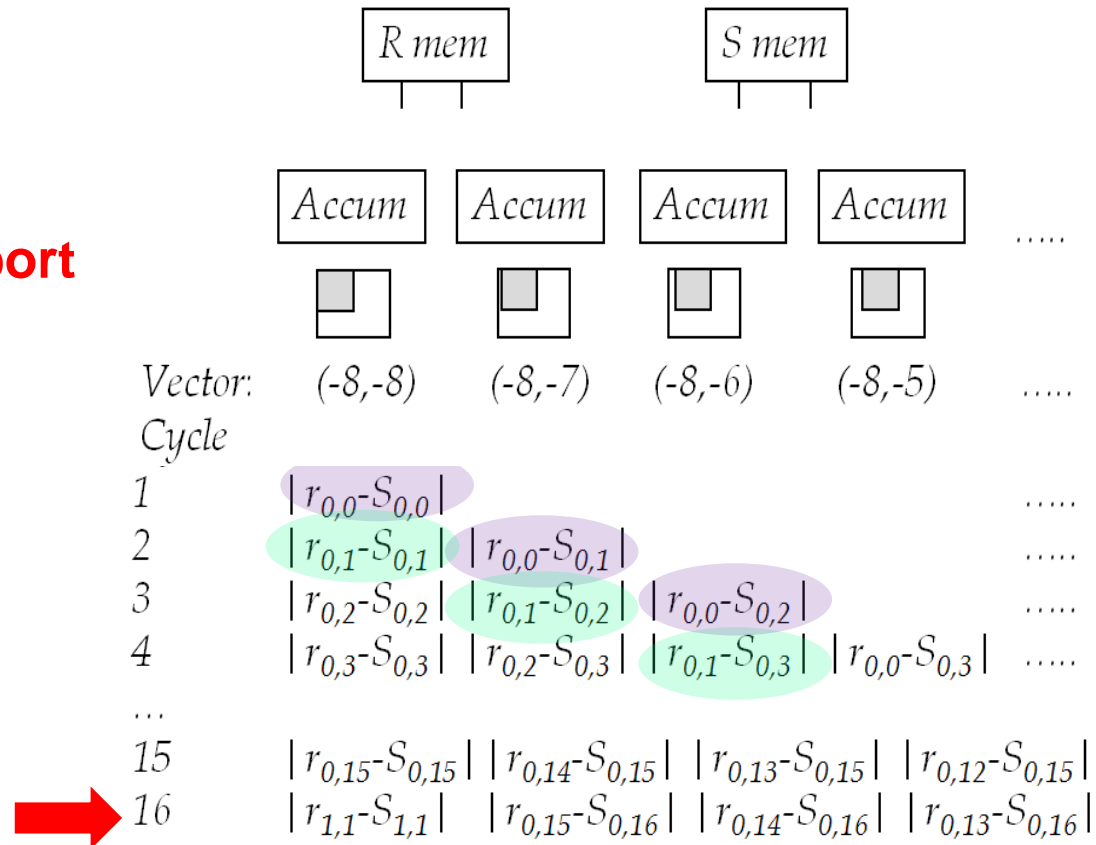

# ... System Design

- ❑ Second Attempt:
  - Stagger Startup of Accumulators

**Problem: Requires 16 port R memory**

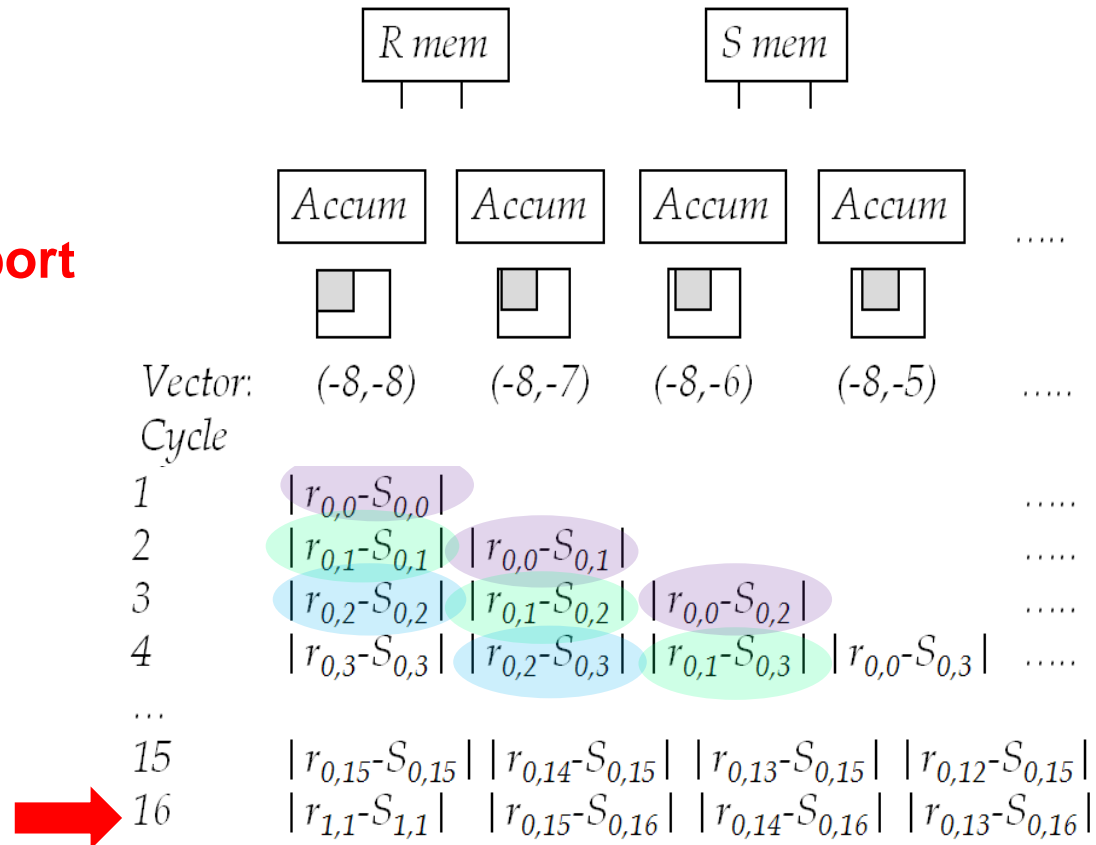


# ... System Design

- ❑ Second Attempt:
  - Stagger Startup of Accumulators


**Problem: Requires 16 port  
R memory**

**Problem: R Pattern**

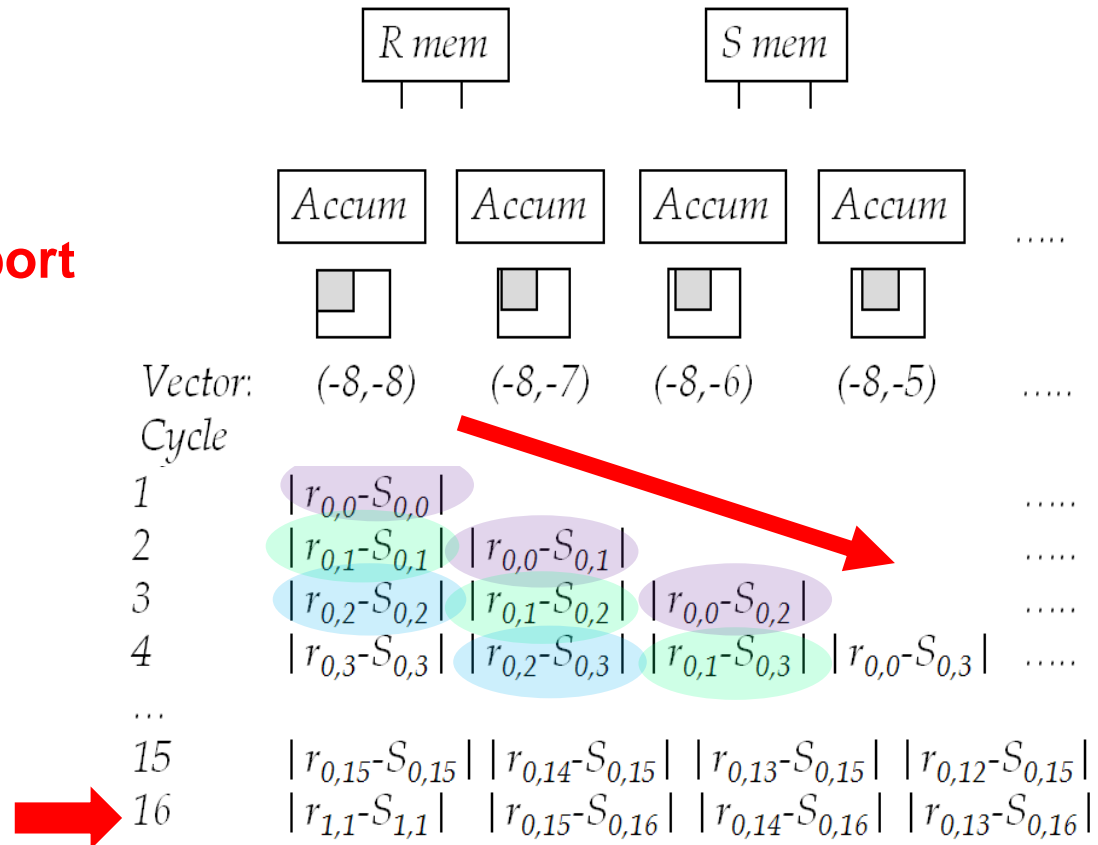
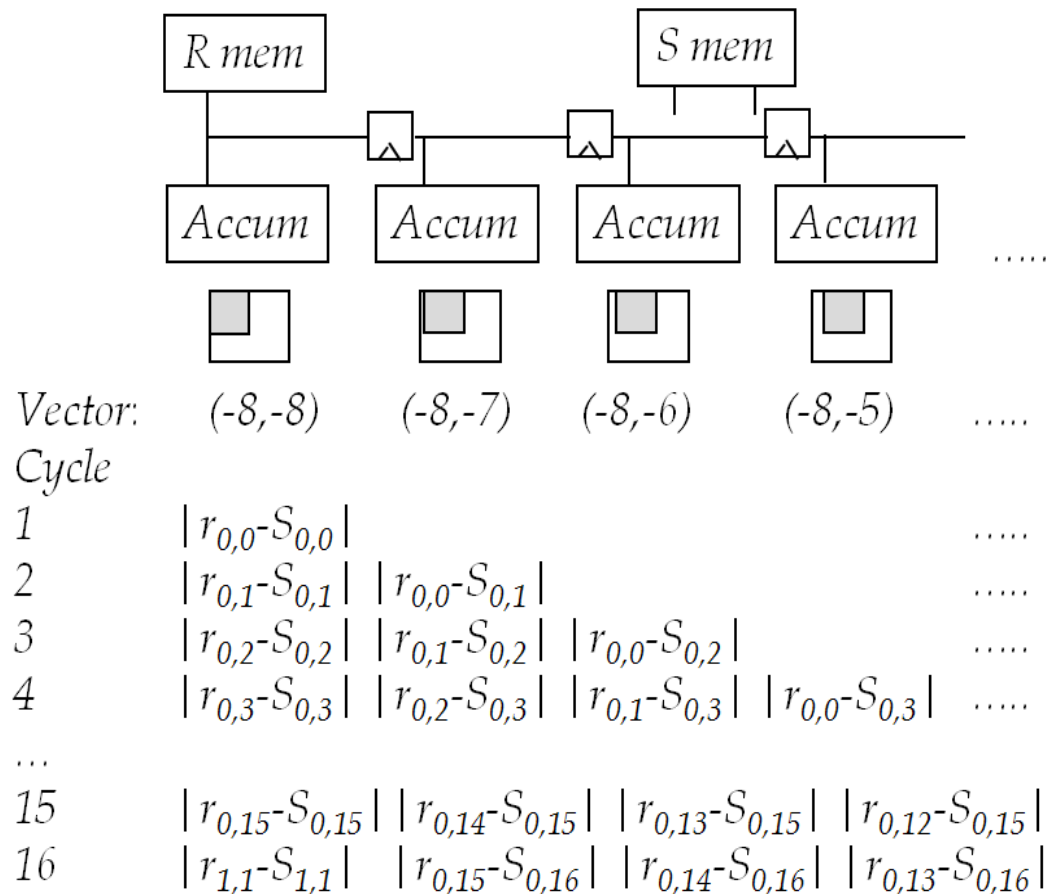
# ... System Design

- Final Solution:
  - Pipeline R
  - Keeps hardware as busy as possible within the constraints of that hardware




2 S mem ports  
required →

# Step 2 : Design Datapath

- Datapath Details:
- Detailed hardware required to implement above

PE = Processing Element

 

# Coding Datapath

- PE: Note, accumulator cant overflow – saturate at FF

```
module PE (clock, R, S1, S2, S1S2mux, newDist, Accumulate, Rpipe);
input clock;
input [7:0] R, S1, S2;// memory inputs
input S1S2mux, newDist;// control inputs
output [7:0] Accumulate, Rpipe;
reg [7:0] Accumulate, AccumulateIn, Difference, Rpipe;
reg      Carry;

always @(posedge clock) Rpipe <= R;
always @(posedge clock) Accumulate <= AccumulateIn;

always @(R or S1 or S2 or S1S2mux or newDist or Accumulate)
begin // capture behavior of logic
    difference = R - S1S2mux ? S1 : S2;
    if (difference < 0) difference = 0 - difference;
// absolute subtraction
    {Carry,AccumulateIn} = Accumulate + difference;
    if (Carry == 1) AccumulateIn = 8'hFF;// saturated
    if (newDist == 1) AccumulateIn = difference;
// starting new Distortion calculation
end
endmodule
```

Motion Estimator Processing Element (PE).




# Coding Datapath

- PE: Note, accumulator cant overflow – saturate at FF

```
module PE (clock, R, S1, S2, S1S2mux, newDist, Accumulate, Rpipe);
input clock;
input [7:0] R, S1, S2; // memory inputs
input S1S2mux, newDist; // control inputs
output [7:0] Accumulate, Rpipe;
reg [7:0] Accumulate, AccumulateIn, Difference, Rpipe;
reg      Carry;

always @(posedge clock) Rpipe <= R;
always @(posedge clock) Accumulate <= AccumulateIn;

always @(R or S1 or S2 or S1S2mux or newDist or Accumulate)
begin // capture behavior of logic
    difference = R - S1S2mux ? S1 : S2;
    if (difference < 0) difference = 0 - difference;
    // absolute subtraction
    {Carry, AccumulateIn} = Accumulate + difference;
    if (Carry == 1) AccumulateIn = 8'hFF; // saturated
    if (newDist == 1) AccumulateIn = difference;
    // starting new Distortion calculation
end
endmodule
```

 

Motion Estimator Processing Element (PE).

# Coding Datapath


- PE: Note, accumulator cant overflow – saturate at FF

```
module PE (clock, R, S1, S2, S1S2mux, newDist, Accumulate, Rpipe);
input clock;
input [7:0] R, S1, S2; // memory inputs
input S1S2mux, newDist; // control inputs
output [7:0] Accumulate, Rpipe;
reg [7:0] Accumulate, AccumulateIn, Difference, Rpipe;
reg      Carry;

always @(posedge clock) Rpipe <= R;
always @(posedge clock) Accumulate <= AccumulateIn;

always @(R or S1 or S2 or S1S2mux or newDist or Accumulate)
begin // capture behavior of logic
    difference = R - S1S2mux ? S1 : S2;
    if (difference < 0) difference = 0 - difference;
    // absolute subtraction
    {Carry, AccumulateIn} = Accumulate + difference;
    if (Carry == 1) AccumulateIn = 8'hFF; // saturated
    if (newDist == 1) AccumulateIn = difference;
    // starting new Distortion calculation
end
endmodule
```

I don't need  
large distortions

 

Motion Estimator Processing Element (PE).

# Coding Datapath

- PE: Note, accumulator cant overflow – saturate at FF

```
module PE (clock, R, S1, S2, S1S2mux, newDist, Accumulate, Rpipe);
input clock;
input [7:0] R, S1, S2; // memory inputs
input S1S2mux, newDist; // control inputs
output [7:0] Accumulate, Rpipe;
reg [7:0] Accumulate, AccumulateIn, Difference, Rpipe;
reg      Carry;

always @(posedge clock) Rpipe <= R;
always @(posedge clock) Accumulate <= AccumulateIn;

always @(R or S1 or S2 or S1S2mux or newDist or Accumulate)
begin // capture behavior of logic
    difference = R - S1S2mux ? S1 : S2;
    if (difference < 0) difference = 0 - difference;
    // absolute subtraction
    {Carry, AccumulateIn} = Accumulate + difference;
    if (Carry == 1) AccumulateIn = 8'hFF; // saturated
    if (newDist == 1) AccumulateIn = difference;
    // starting new Distortion calculation
end
endmodule
```

I don't need  
large distortions

NO else? Latch?

Motion Estimator Processing Element (PE).

# Coding Datapath


- PE: Note, accumulator cant overflow – saturate at FF

```
module PE (clock, R, S1, S2, S1S2mux, newDist, Accumulate, Rpipe);
input clock;
input [7:0] R, S1, S2; // memory inputs
input S1S2mux, newDist; // control inputs
output [7:0] Accumulate, Rpipe;
reg [7:0] Accumulate, AccumulateIn, Difference, Rpipe;
reg      Carry;

always @(posedge clock) Rpipe <= R;
always @(posedge clock) Accumulate <= AccumulateIn;

always @(R or S1 or S2 or S1S2mux or newDist or Accumulate)
begin // capture behavior of logic
    difference = R - S1S2mux ? S1 : S2;
    if (difference < 0) difference = 0 - difference;
    // absolute subtraction
    {Carry, AccumulateIn} = Accumulate + difference;
    if (Carry == 1) AccumulateIn = 8'hFF; // saturated
    if (newDist == 1) AccumulateIn = difference;
    // starting new Distortion calculation
end
endmodule
```

I don't need  
large distortions

 


NO else? Latch?

No! It always takes a value!!

Motion Estimator Processing Element (PE).

# ... Datapath

## ❑ Comparator:

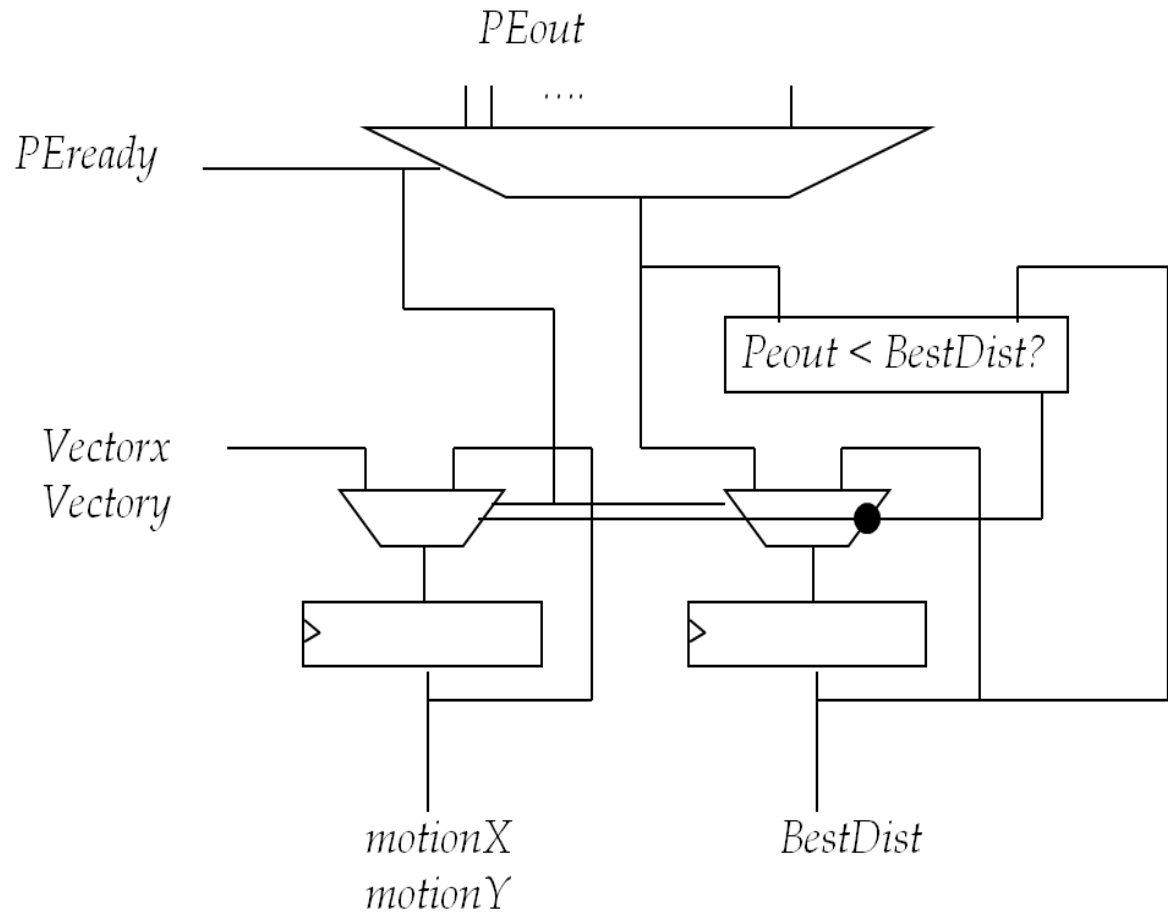

# Datapath

```
module Comparator (clock, CompStart, PEout, PErready, vectorX,
                  vectorY, BestDist, motionX, motionY);
input clock;
input CompStart; // goes high when distortion calculations start
input [8*16:0] PEout; // Outputs of PEs as one long vector
input [15:0] PErready; // Goes high when that PE has a new distortion
input [3:0] vectorX, vectorY; // Motion vector being evaluated
output [7:0] BestDist; // Best Distortion vector so far
output [3:0] motionX, motionY; // Best motion vector so far
reg [7:0] BestDist, newDist;
reg [3:0] motionX, motionY;
reg      newBest;

always @(posedge clock)
    if (CompStart == 0) BestDist <= 8'hFF; //initialize to highest value
    else if (newBest == 1)
        begin
            BestDist <= newDist;
            motionX <= vectorX;
            motionY <= vectorY;
        end

always @(BestDist or PEout or PErready)
    begin
        newDist = PEout [PErready*8+7 : PErready*8];
        if ((!PErready == 0) || (start == 0)) newBest = 0; // no PE is ready
        else if (newDist < BestDist) newBest = 1;
        else newBest = 0;
    end

endmodule
```

Comparator Module.

# Step 3. Identify Control Points

---

## PE control lines:

- ❑ S1S2mux [15:0]; // S1-S2 mux control
- ❑ NewDist [15:0] ; // =1 when PE is starting a new distortion calculation

## Comparator control lines:

- ❑ CompStart;11 = // when PEs running
- ❑ PErady [15:0]; // PErady[I]=1 when PEi has a new distortion vector
- ❑ VectorX [3:0] ;
- ❑ VectorY [3:0];// Motion vector being evaluated

## Memory control lines:

- ❑ Memories organization
- ❑ AddressR [7:0]; // address for Reference memory (0,0). ..(15,15)
- ❑ AddressS1 [9:0] ; // address for first read port of Search mem
- ❑ AddressS2 [9:0] ; // second read port of Search mem (0,0)-(30,30)

# Step. 4 Design Controller

---

- ❑ Best Strategy : Counter
- ❑ Reset Strategy
- Reset needed to initialize entire chip in known state
  - Does not apply here, as long as “start” comes from a unit that does use a reset



# Step. 4 Design Controller

## ❑ Best Strategy : Counter

```
always @(posedge clock)
    if (start == 0) count <= 12'b0;
    else if (completed == 0) count <= count + 1'b1;

always @(count)
    begin
        for (i=0; i<15; i = i+1)
            begin
                NewDist[i] = (count[7:0] == i);
                PReady[i] = (NewDist[i] && !(count < 9'd256));
                S1S2mux[i] = (count[3:0] > i);
            end
        AddressR = count[7:0];
        AddressS1 = (count[11:8] + count[7:4]>>4)*5'd32 + count[3:0];
        AddressS2 = (count[11:8] + count[7:4]>>4)*4'd16 + count[3:0];
        VectorX = count[3:0] - 4'd7;
        VectorY = count[11:8]>>4 - 4'd7;
        complete = (count = 4'd16 * (9'd256 + 1));
    end

endmodule
```

# Step. 4 Design Controller

## ❑ Best Strategy : Counter

```
module control (clock, start, S1S2mux, NewDist, CompStart, PErready,
                VectorX, VectorY, AddressR, AddressS1, AddressS2);
input clock;
input start; // = 1 when`going`
output [15:0] S1S2mux;
output [15:0] NewDist;
output CompStart;
output [15:0] PErready;
output [3:0] VectorX, VectorY;
output [7:0] AddressR;
output [9:0] AddressS1, AddressS2;
reg [15:0] S1S2mux;
reg [15:0] NewDist;
reg CompStart;
reg [15:0] PErready;
reg [3:0] VectorX, VectorY;
reg [7:0] AddressR;
reg [9:0] AddressS1, AddressS2;
reg [12:0] count;
reg completed;
integer i;
```